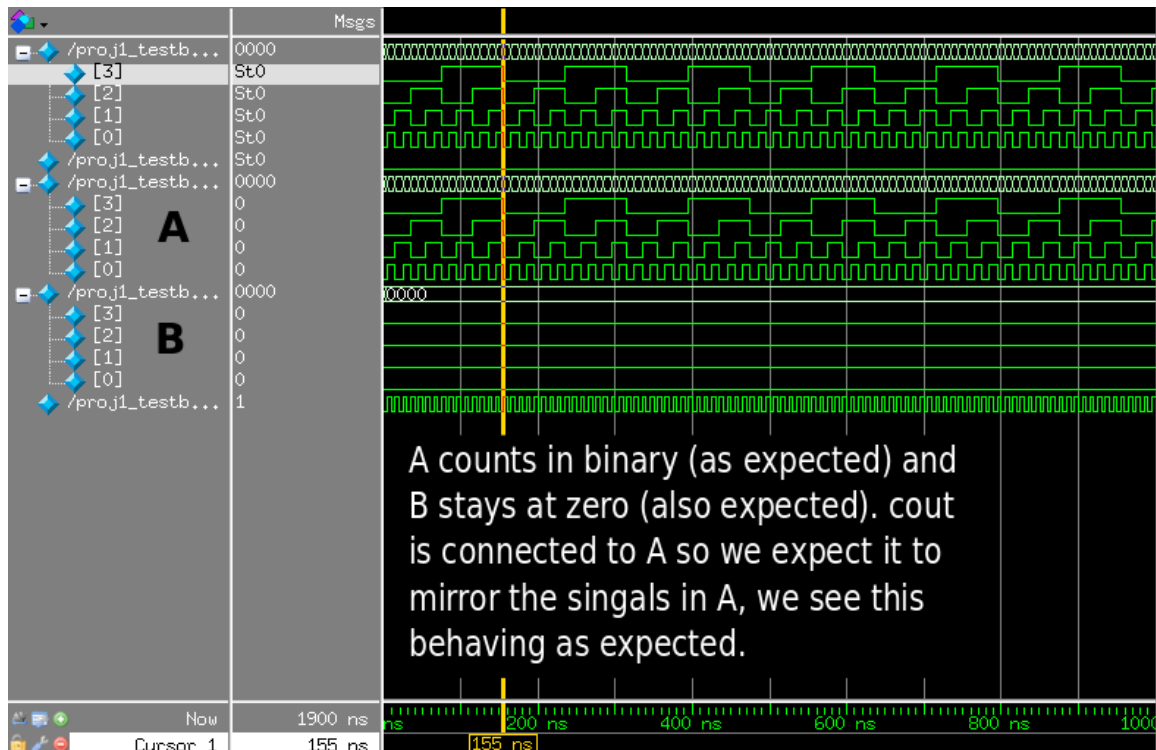


Lab Report

1. Collect your waveform timing diagram for the circuit along with your finished, correct Verilog code into one document. Annotate your simulation diagrams with notes/labels to explain what is being tested.



2. Lab Code

```

module flipflop(reset, clk, d_in, d_out);
    input reset, clk;
    input d_in;
    output d_out;
    reg d_out;

    always @(posedge clk)
    begin

        if (reset)
            d_out <= 0;
        else
            d_out <= d_in;
        end
    endmodule

module fulladder(a, b, cin, sum, cout);
    input a, b, cin;
    output sum, cout;

    assign sum = a ^ b ^ cin;
    assign cout = a & b | a & cin | b & cin;
endmodule

module mux(in_a, in_b, sel, out);

```

```
input in_a, in_b;
input sel;
output out;
reg out;

always @(in_a or in_b or sel)
begin
    case (sel)
        1'b0: out = in_a;
        1'b1: out = in_b;
    endcase
end
endmodule

module ripple_adder(a, b, sum, cout);
    input [3:0] a, b;
    output [3:0] sum;
    output cout;

    wire [3:0] c;
    assign c[0]=0;

    fulladder f0(a[0], b[0], c[0], sum[0], c[1]);
    fulladder f1(a[1], b[1], c[1], sum[1], c[2]);
    fulladder f2(a[2], b[2], c[2], sum[2], c[3]);
    fulladder f3(a[3], b[3], c[3], sum[3], cout);
endmodule

module proj1_testbench;

    wire [3:0] sum;
    wire cout;

    reg [3:0] A, B;
    reg clk;

    // DUT = Device under test
    ripple_adder DUT(A, B, sum, cout);

    always
        #5 clk=~clk;

    initial begin
        clk = 1'b0;
        A = 8'h00;
        B = 8'h00;
    end

    always @(posedge clk)
    begin
        A = A + 1;
    end
endmodule
```

3. Finally, indicate your estimate of the amount of time you spent on this project, what you felt was most valuable and least valuable about this project, and any suggestions you might have for improving this project in the future.

I spent about 3 hours on this. I have never written any Verilog so most of the time I spent on this project was spent learning how to use and operate modelsim.